

Institute of Engineering  
Jiwaji University

Unit-IV BE IV Sem  
Transmission Line Analogy (Part-I)  
EL-402 ELECTRONICS

Submitted By:  
Swati Dixit  
Electronics Dept.

## Topic - Transmission lines

Introduction :- Transmission lines are used to transmit electric energy and signals from one point to another specially from a source to load load.

ex:- hydrogeneratic plant, Stereo System, Cable service provider and T.V set.

In short some examples for higher frequencies as devices on a circuit board are less familiar.

Negligible length  
Time delay (distances large)

Note: Wave phenomena on transmission lines, we have point-to-point energy propagation in free space or in dielectrics.

Network :-

- 1) Lumped Network → The basic element in the circuit resistor, capacitors, inductors and the connection between them. They are considered lumped elements if the time delay in the traversing the elements is negligible.
- 2) Distributed Network → If the interconnections are large enough. They (resistive, capacitive and inductive

characteristics must be evaluated on per-unit-distance basis.

## TRANSMISSION - LINE EQUATIONS →

The differential equations which the voltage or current must satisfy on a uniform transmission line.

### Methods :-

- i) Maxwell's equations subject to the boundary conditions imposed by the particular transmission line.
- 2) TEM-wave problem once and for all for any two-conductors transmission line having lossless conductors.

### Voltage & Current Equation →

The inductance, capacitance, shunt conductance, and series resistance associated with an incremental length of line.

Let us do assume in terms of a coaxial transmission line containing a dielectric of permeability  $\mu$ , permittivity  $\epsilon'$ , and conductivity  $\sigma$ . The inner and outer conductors have a high conductivity  $\sigma_c$ .


Let us again assume propagation in the  $a_z$  direction. Cut out a section of length  $\Delta z$  containing a resistance  $R\Delta z$ , an inductance  $L\Delta z$ , a conductance  $G\Delta z$ , and a capacitance  $C\Delta z$ .

The voltage  $V$  between conductors is in general a function of  $z$  and  $t$ , as

$$V(z, t) = V_0 \cos(\omega t - \beta z + \psi)$$

We may use Euler's identity to express this in complex notation,
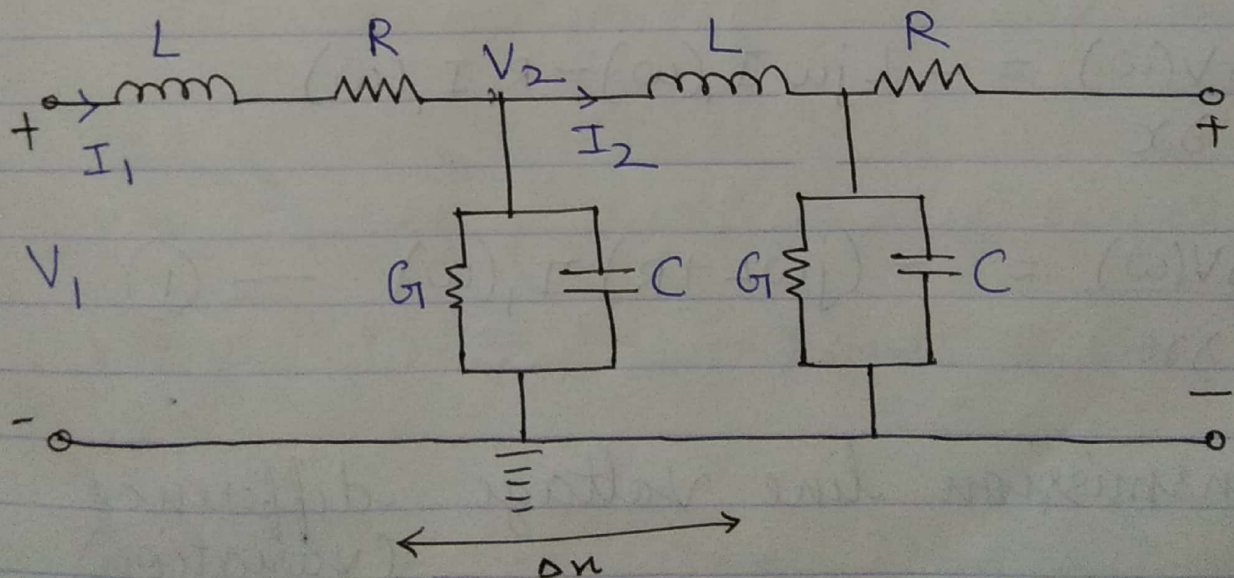
$$\begin{aligned} V(z, t) &= \text{Re} \{ V_0 e^{j(\omega t - \beta z + \psi)} \} \\ &= \text{Re} \{ V_0 e^{j\psi} e^{-j\beta z} e^{j\omega t} \} \quad \text{--- (A)} \end{aligned}$$



$$\begin{aligned} \Delta V &= V_2 - V_1 \\ \Delta I &= I_2 - I_1 \end{aligned}$$

## Voltage Equation

$$V_2 = V_1 - L \frac{\Delta x dI_1}{dt} - R \Delta x I_1$$

$$\Delta V \Rightarrow$$

$$V_2 - V_1 = -L \frac{\Delta x dI_1}{dt} - R \Delta x I_1$$

$$\frac{\Delta V}{\Delta x} = -L \frac{dI_1}{dt} - R I_1$$

$$\frac{\partial V}{\partial x} = -L \frac{dI_1}{dt} - R I_1$$

Laplace transformation

$$\frac{\partial V(s)}{\partial x} = -L s I_1(s) - R I_1(s)$$

$$\frac{\partial V(\omega)}{\partial x} = -L j\omega I_1(\omega) - R I_1(\omega)$$

$$\frac{\partial V(\omega)}{\partial x} = -(j\omega L + R) I_1(\omega) \quad \text{--- (1)}$$

\* Transmission line voltage difference (variation) with respect to distance.

$$\frac{\partial V(\omega)}{\partial x} = -(j\omega L + R) I_1(\omega) \quad - (1)$$

$$\begin{cases} I_1 = I \\ V_1 = V \end{cases}$$

$$\frac{\partial V}{\partial x} = -(j\omega L + R) I$$

$$\boxed{\frac{\partial V}{\partial x} = -(R + j\omega L) I} \quad - (1)$$

$$= -Z I$$

$$\begin{aligned} \Delta &\sim 0 \\ I_1 &\approx I_2 \\ V_1 &\approx V_2 \end{aligned}$$

Rate of change of voltage w.r.t to distance in terms of current.  
Current Equation

$$I_1 - I_c = V_2 G \Delta x + C \Delta x \frac{dV_2}{dt}$$

$$-\Delta I = \left( V_2 G + C \frac{dV_2}{dt} \right) \Delta x$$

$$\frac{\Delta I}{\Delta x} = - \left( V_2 G + C \frac{dV_2}{dt} \right)$$

$$V G = I$$

$$I = C \frac{dV}{dt}$$

$$\frac{\partial I(\omega)}{\partial x} = - \left( V_2(\omega) G + j\omega C V_2(\omega) \right)$$

$$\frac{\partial I(\omega)}{\partial x} = - (G + j\omega C) V_2(\omega)$$

$$\boxed{\frac{\partial I}{\partial x} = - (G + j\omega C) V} \quad - (2)$$

$$= -Y V$$

## Propagation Constant :-

$$\frac{\partial^2 V}{\partial x^2} = -(R + j\omega L) \frac{\partial I}{\partial x}$$
$$= -(R + j\omega L) - (G + j\omega C) V$$

$$\frac{\partial^2 V}{\partial x^2} = (R + j\omega L)(G + j\omega C) V$$

$$\frac{\partial^2 V}{\partial x^2} = \gamma^2 V$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$\gamma$  = propagation constant

## Attenuation Constant & Phase Constant

$$\frac{\partial^2 I}{\partial x^2} = (R + j\omega L)(G + j\omega C) I$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$= \alpha + j\beta$$

$\alpha$  = Attenuation Constant

$\beta$  = Phase Constant