

Institute of Engineering
Jiwaji University

Unit-IV BE IV Sem
Transmission Line Analogy (Part-II)
EL-402 ELECTRONICS

Submitted By:
Swati Dixit
Electronics Dept.

Now,

$$\alpha + j\beta = \gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$= \sqrt{j^2 \omega^2 LC \left(1 + \frac{R}{j\omega L}\right)^{\frac{1}{2}} \left(1 + \frac{G}{j\omega C}\right)^{\frac{1}{2}}}$$

By Taylor Macmillian series

$$(1+x)^{\frac{1}{2}} = 1 + \frac{x}{2} - \frac{x^2}{8}$$

Now, separate real & imaginary
 $x \ll 1$ higher times ignore

$$\gamma = j\omega \sqrt{LC} \left[1 + \frac{R}{2j\omega L} + \frac{R^2}{8\omega^2 L^2} \right] \left[1 + \frac{G}{2j\omega C} + \frac{G^2}{8\omega^2 C^2} \right]$$

$$j\omega \sqrt{LC} \left[1 + \frac{G^2}{8\omega^2 C^2} - \frac{RG}{G\omega^2 LC} + \frac{R^2}{8\omega^2 L^2} \right]$$

$$+ \frac{R^2 G^2}{64 \omega^2 L^2 C^2} + \frac{G}{2j\omega C} + \frac{R}{2j\omega L}$$

$$\left. + \frac{RG^2}{16j\omega^3 C^2} + \frac{R^2 G}{16\omega^2 L^2 C} \right]$$

$$\omega\sqrt{LC} \left(\frac{G}{2\omega C} + \frac{R}{2\omega L} + \frac{RG^2}{16\omega^3 LC^2} + \frac{R^2 G}{16\omega^3 L^2 C} \right) + j \left(1 + \frac{G^2}{8\omega^2 C^2} - \frac{RG}{4\omega^3 LC} + \frac{R^2}{8\omega^2 L^2} + \frac{R^2 G^2}{64\omega^4 L^2 C^2} \right)$$

$$\omega\sqrt{LC} \left\{ \left[\frac{G}{2\omega C} + \frac{R}{2\omega L} \right] + j \left[1 + \frac{G^2}{8\omega^2 C^2} - \frac{RG}{4\omega^3 LC} + \frac{R^2}{8\omega^2 L^2} \right] \right\}$$

powers more than 3 are ignored

Real part

$$\alpha = \frac{1}{2} \left(\frac{G\sqrt{LC}}{\sqrt{L} \sqrt{C}} + \frac{R\sqrt{LC}}{\sqrt{L} \sqrt{C}} \right) \quad \Bigg| \quad Z = \sqrt{\frac{L}{C}} \Omega$$

$$\alpha = \frac{1}{2} \left(G \sqrt{\frac{L}{C}} + R \sqrt{\frac{C}{L}} \right)$$

$$\beta = \omega \sqrt{LC} \left[1 + \frac{1}{8} \left\{ \left(\frac{G}{\omega C} \right)^2 - \frac{2RG}{\omega^2 LC} + \left(\frac{R}{\omega L} \right)^2 \right\} \right]$$

$$\beta = \omega \sqrt{LC} \left[1 + \frac{1}{8} \left(-\frac{G}{\omega C} + \frac{R}{\omega L} \right)^2 \right]$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

for, loss less transmission
 $R=0, G=0$

$$\gamma = j\omega L + j\omega C$$

$$= 0 + j\omega \sqrt{LC}$$

$$\alpha + j\beta$$

$$\alpha = 0$$

$$\beta = \omega \sqrt{LC}$$

By dropping in A.P.E. of suppressing $e^{j\omega t}$ we transform the voltage to a phasor, which is denoted by an 's' subscript,

$$V_s(z) = V_0 e^{j\psi} e^{-j\beta z}$$

Now eqⁿ (1) & (2) can be written as,

Δz — approach zero

ΔI — approach zero

$$\frac{dV_s}{dz} = -(R + j\omega L) I_s \quad \text{--- (3)}$$

$$\frac{dI_s}{dz} = -(G + j\omega C) V_s \quad \text{--- (4)}$$

By comparing with Maxwell's curl equations for the uniform plane wave in conducting medium.

From

$$\nabla \times E_s = -j\omega \mu H_s$$

$$E_s = E_{xs} a_x$$

$$H_s = H_{ys} a_y$$

we set $E_s = E_x a_x$ & $H_s = H_y a_y$,

E_x & H_y are functions of z only

to obtain a scalar eqⁿ we find analogous to (3) & (4)

$$\frac{dE_x}{dz} = -j\omega\mu H_y$$

$$\nabla \times H_s = (\sigma + j\omega\epsilon') E_s$$

$$\frac{dH_y}{dz} = -(\sigma + j\omega\epsilon') E_x$$

The boundary conditions on V_s & E_x are same there I_s & H_y .

Note :- From it two circuit equations may be obtained from a knowledge of the solution of the two field equations,

$$E_x = E_{x0} e^{-jkz}$$

we obtain voltage equation

$$V_s = V_0 e^{-\gamma z}$$

Now, the wave propagates in +z direction with an amplitude

$$V = V_0 \text{ at } z=0, t=0 \text{ for } y=0.$$

The propagation constant for the uniform plane wave,

$$jk = \sqrt{j\omega\mu(\sigma + j\omega\epsilon')}$$

$$\text{becomes } \gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\text{The wavelength } \lambda = \frac{2\pi}{\beta}$$

$$\text{Phase velocity } v_p = \frac{\omega}{\beta}$$

of this expression is valid both for the uniform plane wave of transmission line. For a lossless line ($R = G = 0$) we see that

$$\gamma = j\beta = j\omega\sqrt{LC}$$

hence,

$$v_p = 1/\sqrt{LC}$$

From the expression for magnetic field intensity,

$$H_{ys} = \frac{E_{xo}}{\eta} e^{-jkz}$$

We see that the positively travelling current wave

$$I_s = \frac{V_0}{Z_0} e^{-\gamma z}$$

As equation (1) & (2)

$$\frac{\partial V}{\partial x} = -(R + j\omega L)I = -ZI$$

$$\frac{\partial I}{\partial x} = -(G + j\omega C)V = -yV$$


$$\frac{\partial^2 V}{\partial x^2} = \gamma^2 V, \quad \frac{\partial^2 I}{\partial x^2} = \gamma^2 I$$

$$V = Ae^{-\gamma x} + Be^{+\gamma x}$$

$$I = Ce^{-\gamma x} + De^{+\gamma x}$$

$$V_i(x) = Ae^{-\gamma x}$$

$$I_i(x) = Ce^{-\gamma x}$$

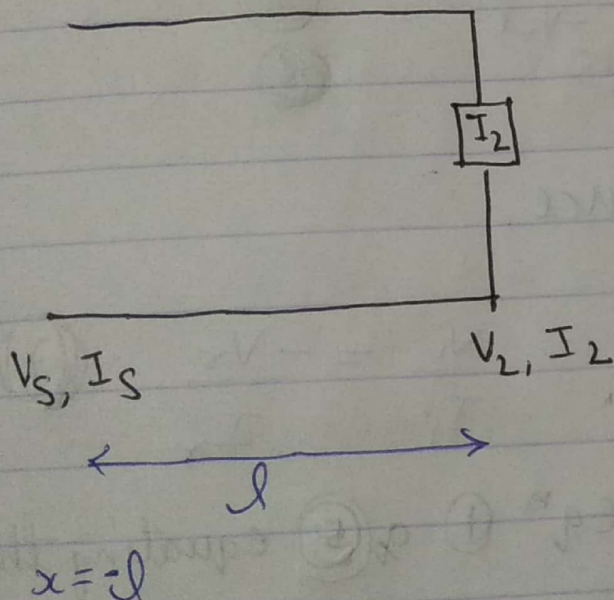

To find C.F & P.I
in this condition
only C.F

$$\frac{d^2 y}{dx^2} - a^2 y = 0$$

$$m^2 - a^2 = 0$$

$$m = \pm a$$

$$y = C_1 e^{-ax} + C_2 e^{ax}$$

$$V_r(x), I_r(x)$$

$$V_r(x) = Be^{+\gamma x}$$

$$I_r(x) = De^{+\gamma x}$$

$$\begin{aligned}
 V_i(0) &= A = V_i & \text{vtg at load} \\
 I_i(0) &= C = I_i \\
 V_r(0) &= B = V_r \\
 I_r(0) &= D = I_r
 \end{aligned}$$

$$V(x) = V_i e^{-\gamma x} + V_r e^{+\gamma x}$$

$$V(x) = V_i e^{-\gamma x} + V_r e^{+\gamma x} \quad (5)$$

$$I(x) = I_i e^{-\gamma x} + I_r e^{+\gamma x} \quad (6)$$

$$V(0) = V_2 = V_i + V_r$$

$$I(0) = I_2 = I_i + I_r$$

$$V(-l) = V_s = V_i e^{\gamma l} + V_r e^{-\gamma l} \quad (7)$$

$$I(-l) = I_s = I_i e^{\gamma l} + I_r e^{-\gamma l} \quad (8)$$

Now, Characteristic impedance,

$$Z_0 = \frac{V_i}{I_i} = \frac{V_i e^{-\gamma x}}{I_i e^{-\gamma x}} = \frac{V_i}{I_i} = -\frac{V_r}{I_r} \quad (9)$$

Differentiate eqⁿ (5), w by eqⁿ (1) w (5) equating them

$$-\gamma V_i e^{-\gamma x} + \gamma V_r e^{+\gamma x} = -(R + j\omega L) I$$

$$\text{Putting value from (7)} = -Z(I_i e^{-\gamma x} + I_r e^{+\gamma x})$$

$$+\gamma Z_0 (I_i e^{-\gamma x} + I_r e^{+\gamma x}) = +Z (I_i e^{-\gamma x} + I_r e^{+\gamma x})$$

$$Z_0 = \frac{Z}{Y} = \frac{R + j\omega L}{\sqrt{(R + j\omega L)(G + j\omega C)}}$$

$$Z_0 = \frac{\sqrt{R + j\omega L} \sqrt{R + j\omega L}}{\sqrt{(R + j\omega L)(G + j\omega C)}}$$

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

Loss less transmission

$$R = 0, \quad G = 0$$

$$Z_0 = \sqrt{\frac{L}{C}} \Omega$$

$$Y = j\omega\sqrt{LC} = \alpha + j\beta \quad | \quad \alpha = 0$$

$$\beta = \omega\sqrt{LC}$$

$$Y = j\beta$$

$$A + jB = |I| e^{j\theta}$$


Input Impedance

$$Z_{in} = \frac{V_s}{I_s} = \frac{V_i e^{j\beta l} + V_r e^{-j\beta l}}{I_i e^{j\beta l} + I_r e^{-j\beta l}}$$

$$= \frac{V_i e^{j\beta l} + V_r e^{-j\beta l}}{I_i e^{j\beta l} + I_r e^{-j\beta l}}$$

$$= \frac{I_i Z_0 e^{j\beta l} - I_r Z_0 e^{-j\beta l}}{I_i e^{j\beta l} + I_r e^{-j\beta l}} = Z_0 \left[\frac{I_i e^{j\beta l} - I_r e^{-j\beta l}}{I_i e^{j\beta l} + I_r e^{-j\beta l}} \right]$$

from eqⁿ - (9) eqⁿ

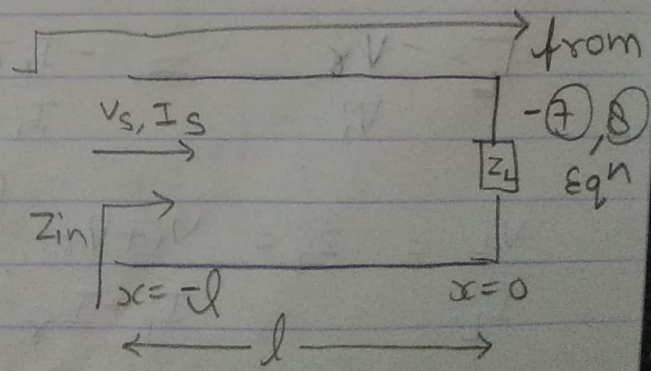

REFLECTION COEFFICIENT

from Eqⁿ (9)

$$\frac{-V_r}{I_r} = \frac{V_i}{I_i} = Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}}$$

$$Y = \sqrt{(R+j\omega L)(G+j\omega C)}$$

$$\Gamma = \frac{V_r}{V_i} \Rightarrow \Gamma(x) = \frac{V_r(x)}{V_i(x)}$$

Γ = Reflection Coefficient

$$\Gamma_L(x) = \frac{V_r(x)}{V_i(x)} = \frac{V_r e^{\gamma x}}{V_i e^{-\gamma x}} = \frac{V_r}{V_i} e^{-2\gamma x}$$

Voltage Reflection Coefficient

As, we know

$$\frac{V_i}{I_i} = Z_0, \quad \frac{V_r}{I_r} = -Z_0$$

$$\Gamma_L = \frac{V_r}{V_i} = \frac{-I_r Z_0}{I_i Z_0} = -\frac{I_r}{I_i}$$

Current Reflection Coefficient

$$\frac{V_L}{I_L} = Z_L = \frac{V_i + V_r}{I_i + I_r}$$

$$Z_L = \frac{V_i + \Gamma V_i}{I_i - \Gamma I_i} = \frac{V_i}{I_i} \left(\frac{1 + \Gamma}{1 - \Gamma} \right)$$

$$Z_L = \frac{1 + \Gamma}{1 - \Gamma}$$

$$Z_L - Z_L \Gamma = Z_0 + Z_0 \Gamma$$

$$Z_L - Z_0 = (Z_0 + Z_L) \Gamma$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Γ is the reflected voltage to incident voltage.
or Γ is the reflected negative current to incident current.

$$\frac{V_s}{I_s} = \frac{V_i e^{+\gamma l} + V_r e^{-\gamma l}}{I_i e^{+\gamma l} + I_r e^{-\gamma l}}$$

$$= \frac{V_i e^{j\beta l} + V_r e^{-j\beta l}}{I_i e^{j\beta l} + I_r e^{-j\beta l}}$$

$$= \frac{I_i Z_0 e^{j\beta l} - I_r Z_0 e^{-j\beta l}}{I_i e^{j\beta l} + I_r e^{-j\beta l}}$$

$$= Z_0 \left[\frac{I_i e^{j\beta l} - I_r e^{-j\beta l}}{I_i e^{j\beta l} + I_r e^{-j\beta l}} \right]$$

$$= Z_0 \left[\frac{I_i e^{j\beta l} + I_i \Gamma e^{-j\beta l}}{I_i e^{j\beta l} - I_i \Gamma e^{-j\beta l}} \right]$$

$$I_r = -I_i \Gamma$$

$$Z_{in} = Z_0 \left[\frac{e^{j\beta l} + \Gamma e^{-j\beta l}}{e^{j\beta l} - \Gamma e^{-j\beta l}} \right]$$

$$= Z_0 \left[\frac{e^{j\beta l} + \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-j\beta l}}{e^{j\beta l} - \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-j\beta l}} \right]$$

$$Z_0 \left[\frac{Z_L (e^{j\beta l} + e^{-j\beta l}) + Z_0 (e^{j\beta l} - e^{-j\beta l})}{Z_L (e^{j\beta l} - e^{-j\beta l}) + Z_0 (e^{j\beta l} + e^{-j\beta l})} \right]$$

$$Z_{in} = Z_0 \left[\frac{e^{j\beta l} + \Gamma e^{-j\beta l}}{e^{j\beta l} - \Gamma e^{-j\beta l}} \right]$$

$$\sin \theta = \frac{e^{j\theta} - e^{-j\theta}}{2j}$$

$$\cos \theta = \frac{e^{j\theta} + e^{-j\theta}}{2}$$

$$= Z_0 \left(\frac{Z_L 2 \cos \theta + Z_0 j 2 \sin \theta}{Z_L j 2 \sin \theta + Z_0 2 \cos \theta} \right)^2$$

$$Z_{in} = Z_0 \left[\frac{Z_L + Z_0 j \tan \beta l}{Z_0 + Z_L j \tan \beta l} \right]$$

This is in an antenna, the i/p circuit of TV receiver,

Now, characteristic impedance Z_0 that is analogous to η . Since in conducting medium.

$$\eta = \sqrt{\frac{j\omega\mu}{\sigma + j\omega\epsilon}}$$

We have

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

When a uniform ^{plane} wave in medium 1 is incident on the interface with medium 2,

$$\Gamma = \frac{E_{n0}^-}{E_{n0}^+} = \frac{n_2 - n_1}{n_2 + n_1}$$

The fraction of incident wave that is reflected is called the reflection coefficient which the normal incidence is above in ϵ_0^n

Thus the fraction of the incident voltage wave that is reflected by a line with a different characteristic impedance

$$\Gamma = |\Gamma| e^{j\phi} = \frac{V_0^-}{V_0^+} = \frac{Z_{02} - Z_{01}}{Z_{02} + Z_{01}}$$

$Z_{01} \rightarrow$ from medium 1

$Z_{02} \rightarrow$ from medium 2

$$Z_{in} = Z_0 \cdot \frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l}$$

Standing Wave Ratio :-

$$S = \frac{V_{max}}{V_{min}} = \frac{I_{max}}{I_{min}} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

$$I_{max} = V_{max} / Z_0 \quad \& \quad I_{min} = V_{min} / Z_0$$

The input impedance Z_{in} has maxima and minima that occur respectively at the maxima and minima of the voltage and current standing wave,

$$|Z_{in}|_{max} = \frac{V_{max}}{I_{min}} = S Z_0$$

$$|Z_{in}|_{min} = \frac{V_{min}}{I_{max}} = \frac{Z_0}{S}$$

$$\eta = \eta_3 \quad \text{for } z > 0$$

$$\eta = \eta_2 \quad \text{for } z < 0$$


the ratio E_{xs} to H_{ys} at $z = -l$ is

$$\eta_{in} = \eta_2 \frac{\eta_3 \cos \beta_2 l + j \eta_2 \sin \beta_2 l}{\eta_2 \cos \beta_2 l + j \eta_3 \sin \beta_2 l}$$

∴ therefore the input impedance

$$Z_{in} = Z_{o2} \frac{Z_{o3} \cos \beta_2 l + j Z_{o2} \sin \beta_2 l}{Z_{o2} \cos \beta_2 l + j Z_{o3} \sin \beta_2 l}$$

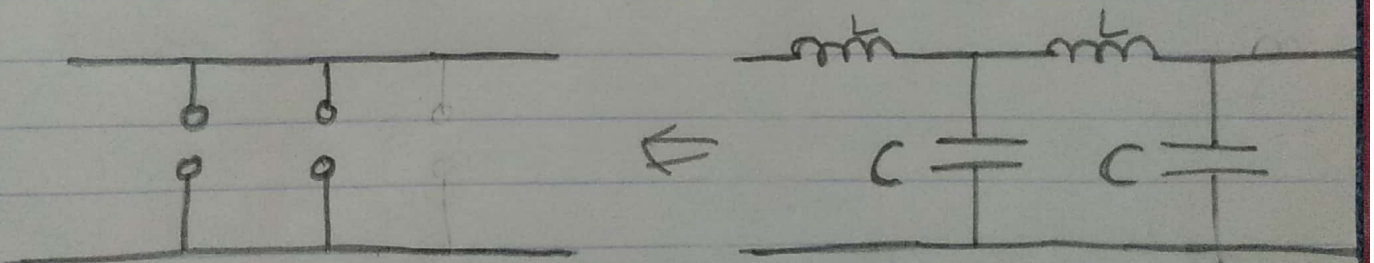Note:- Transmission line at low frequency used in power transmission



Forward path Short Circuit


$$i/p \rightarrow o/p$$

$$\omega \rightarrow 0 \quad X_L = \omega L \rightarrow 0$$

$$X_C = \frac{1}{\omega C} \rightarrow \infty$$

By increasing small it goes straight but not reverse.

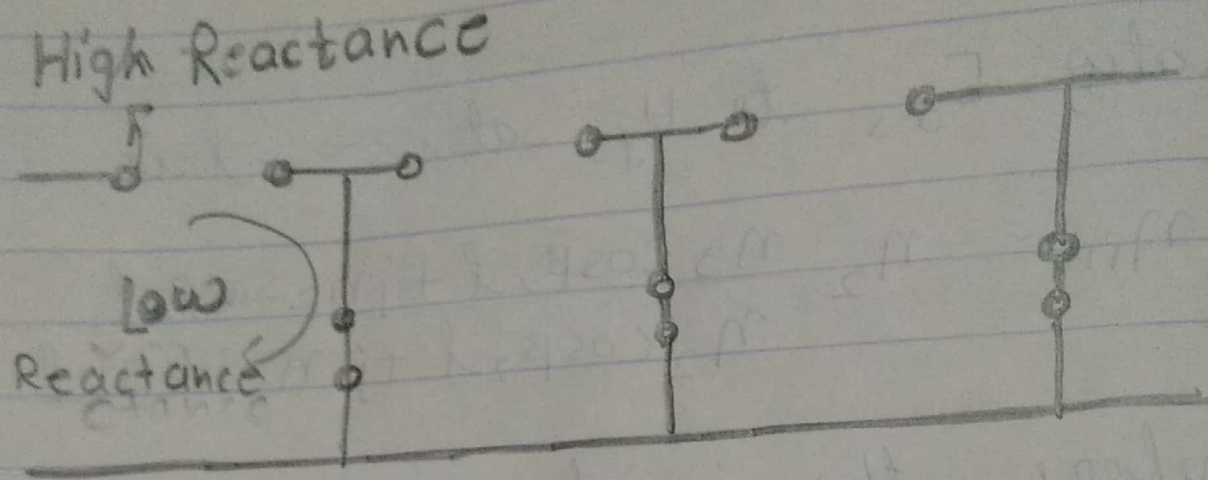Transmission line at higher frequency used in communications.



$$X_L \rightarrow \omega L \rightarrow \infty$$

$$X_C = \frac{1}{\omega C} \rightarrow 0$$